

Measuring -48 V High-Side Current Using the **AD629** Difference Amplifier, **AD8603** Op Amp, **AD780** Reference, and **AD7453** 12-Bit ADC Single-Supply Components

CIRCUIT FUNCTION AND BENEFITS

The -48 V power rail is widely used in wireless base stations and telecommunication equipment. Used in network central offices, the voltage of the power rail can vary between -48 V and -60 V . Measuring the current at these voltages typically requires components that operate on dual supplies, such as $\pm 15\text{ V}$. Typically, only the front-end conditioning amplifiers that interface directly with the -48 V rail use dual supplies. The remainder of the system operates on single supplies. Eliminating the negative

supply reduces complexity and cost. Using the **AD629** and the **AD8603** in the circuit shown in Figure 1 allows users to measure current at -48 V to -60 V while operating only on positive supplies.

Compared with low-side current sensing, high-side current sensing rejects ground noise and can detect short circuits during operation.

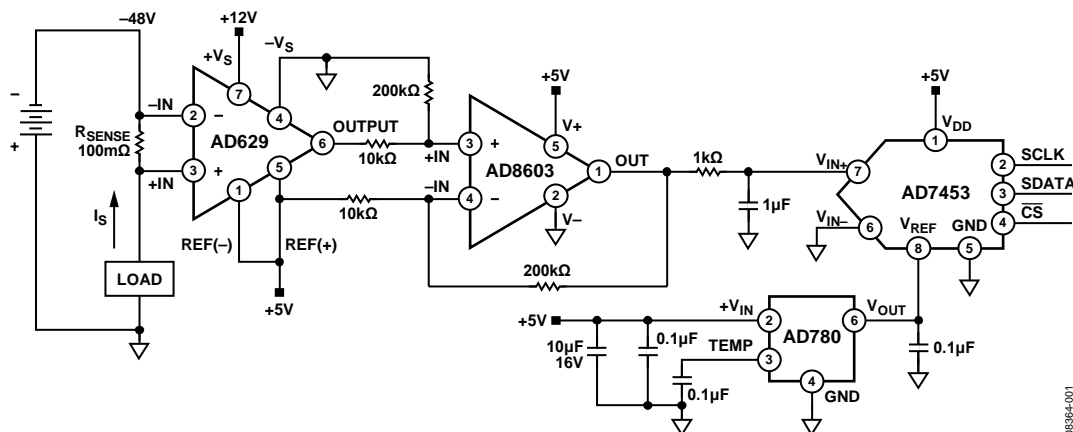


Figure 1. Circuit Used to Measure -48 V Current (Simplified Schematic)

06384-001

TABLE OF CONTENTS

Circuit Function and Benefits.....	1	Common Variations.....	4
Revision History	2	References.....	4
Circuit Description.....	3		

REVISION HISTORY

12/2017—Rev. 0 to Rev. A

Document Title Changed from CN0100 to AN-1531.....	Universal
Changes to Figure 1	1
Changes to Circuit Description Section and Table 1	3

7/2009—Revision 0: Initial Version

CIRCUIT DESCRIPTION

This circuit uses the [AD629](#) difference amplifier to condition voltages beyond its supplies. The minimum and maximum allowable input common-mode voltage is determined by the following equations:

$$V_{COM_MAX} = 20 \times (+V_S - 1.2) - 19 \times V_{REF}$$

$$V_{COM_MIN} = 20 \times (-V_S + 1.2) - 19 \times V_{REF}$$

where:

V_{COM_MAX} is the common-mode voltage, maximum.

$+V_S$ is the positive supply voltage.

V_{REF} is the reference voltage

V_{COM_MIN} is the common-mode voltage, minimum.

$-V_S$ is the negative supply voltage.

When $V_{REF} = 5$ V, $+V_S = 12$ V, and $-V_S = 0$ V, the [AD629](#) common-mode input range is -71 V to $+121$ V. This range is high enough to cover the entire expected range of the -48 V rail. The [AD629](#) difference amplifier senses the differential voltage, sense current (I_S) \times sense resistor (R_{SENSE}), which is generated by the current flowing through the shunt resistor. Because the [AD629](#) has a fixed gain of 1, its output voltage is equal to $I_S \times R_{SENSE} + V_{REF}$.

The shunt resistor is 100 m Ω with 0.1% tolerance and a maximum power rating of 1 W. When selecting the shunt resistor, both current measurement accuracy and self heating effects must be considered.

The [AD8603](#) is configured as a subtractor so that it can reject the 5 V common-mode voltage and amplify the signal of interest, $I_S \times R_S$. The signal is amplified by a factor of 20 to span the 2.5 V full-scale input range of the [AD7453](#) analog-to-digital converter (ADC). A full-scale 2.5 V signal to the ADC corresponds to a current of 1.25 A on the -48 V supply. The [AD8603](#) is selected for this circuit because it has low input bias current, low input offset drift, and rail-to-rail input and output features. The rail-to-rail output allows the [AD8603](#) to share the same supply as the ADC. Note that the output of the [AD8603](#) can only decrease to approximately 50 mV above ground due to its output stage. This output corresponds to a sense current, I_S , of about 25 mA. Therefore, currents less than about 25 mA cannot be measured. However, accuracy for very low currents is not usually required.

The ratios of the four resistors that form the subtractor must be matched to obtain maximum common-mode rejection (CMR). In this stage, the subtractor has to reject the 5 V common-mode signal from the [AD629](#).

The [AD7453](#) 12-bit ADC is used because of its pseudo differential input that can simplify the interface between the [AD8603](#) and the ADC. In addition, its small package and low cost make it useful in cost sensitive or size limited cases.

The [AD780](#) is used as the voltage reference for the [AD7453](#) 12-bit ADC because of its accuracy and ease of use.

The circuit was tested by measuring the digitized output voltage as a function of current for supply rails of -48 V and -60 V. The results shown in Figure 2 demonstrate a close correlation to the expected values and good linearity under different common-mode voltages.

The error due to the CMR of the [AD629](#) is the largest error. The total offset error is amplified by the signal gain of the [AD8603](#) difference amplifier, 20; therefore, the total offset error can be as high as 156 mV referenced to the [AD8603](#) output.

This calculation shows that the CMR of the input difference amplifier is important for low offset. If the current sense circuit is used outdoors, the temperature specifications (initial gain drift, offset voltage drift, and CMR over the entire temperature range) are important, and the [AD629](#) is ideal for such applications.

The [AD8603](#) contributes an error caused by its input offset voltage (0.3 mV maximum) and input bias current (1 pA). These amplifier errors produce a maximum output offset error of about 6.3 mV for the noise gain of 21. The total maximum output offset error is the sum of the error due to the [AD629](#) (156 mV) and the [AD8603](#) (6.3 mV), or 162.3 mV referred to the [AD8603](#) output. Remove this error with system calibration.

If using the typical specifications rather than maximums, the offset voltage at the [AD8603](#) output is approximately 45 mV.

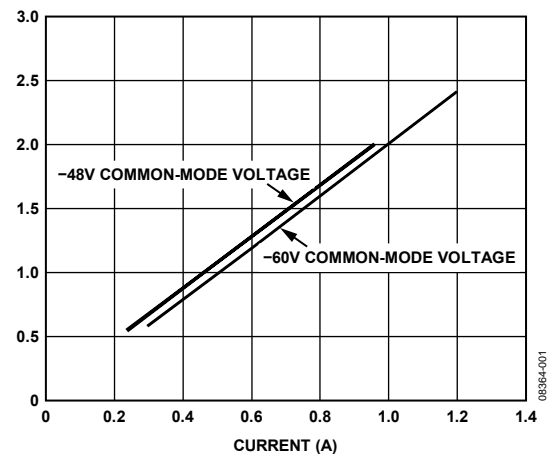


Figure 2. Digitized Output Voltage vs. Current for Common-Mode Voltages of -48 V and -60 V

The offset errors of the [AD629A](#) are shown in Table 1 and can be calculated as follows using the maximum specifications.

Table 1. [AD629A](#) DC Errors

Error Source ¹	Error Voltage (mV)
Initial Gain Error	0.05
Offset Voltage	1
DC CMR (77 dB)	6.768

¹ The total offset error voltage of these error sources is 7.818 mV.

The circuit must be constructed on a multilayer printed circuit board with a large area ground plane. Proper layout, grounding, and decoupling techniques must be used to achieve optimum performance (see the [MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of “AGND” and “DGND”*](#) and [MT-101 Tutorial, *Decoupling Techniques*](#)).

COMMON VARIATIONS

The [ADR361](#) is another option for the voltage reference because of its smaller size, low power, and high precision.

An integrated instrumentation amplifier, such as the [AD8223](#) or [AD8226](#), can be used instead of the [AD8603](#). This amplifier eliminates the need for the external resistor matching required by the [AD8603](#) circuit. A difference amplifier, such as the [AD8276](#) with integrated resistors, can also be used instead of the [AD8603](#) if a gain of 1 is acceptable.

The [AD629B](#) has a CMR that is 9 dB higher than the [AD629A](#). Its offset voltage is half and its gain error is almost half that of the [AD629A](#). These specifications are critical for cases where system calibration is impossible.

If a more integrated solution is needed for the converter, the [ADuC7019](#), [ADuC7020](#), [ADuC7021](#), [ADuC7022](#), [ADuC7024](#), [ADuC7025](#), [ADuC7026](#), [ADuC7027](#), and [ADuC7028](#) series of ARM7TDMI® precision analog microcontrollers with the integrated 12-bit, 1 MSPS ADC are ideal choices.

REFERENCES

Kitchin, Charles and Lew Counts. 2006. *A Designer's Guide to Instrumentation Amplifiers (3rd Edition)*. Analog Devices.

[MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of “AGND” and “DGND”*](#). Analog Devices.

[MT-035 Tutorial, *Op Amp Inputs, Outputs, Single-Supply, and Rail-to-Rail Issues*](#). Analog Devices.

[MT-061 Tutorial, *Instrumentation Amplifier \(In-Amp\) Basics*](#). Analog Devices.

[MT-068 Tutorial, *Difference and Current Sense Amplifiers*](#). Analog Devices.

[MT-101 Tutorial, *Decoupling Techniques*](#). Analog Devices.